

# Lab 3

Ana Cardenas Beltran

SID: 862158699

Session 23

ENGR ID: acardenasbeltra

UCR NetID: acard079

## Summary

In this lab, I learned how to do parasitic extractions of layouts by running LPE on Custom Designer. I also learned how to design a ring oscillator using hierarchical design. I learned how to connect the inverters to create the ring oscillator and gained more familiarity with running DRC and LVS to verify layouts. Next, I learned how to create a layout from a schematic and designed a layout for a 1-bit full adder and then a 4-bit full adder using hierarchical design. A large part of this lab was practicing debugging with the DRC and LVS as well.

## Checkoff Video

Week 1: <https://youtu.be/SzEygGEC7ds>

Week 2&3: <https://youtu.be/3hqNZoSdNoU>

## Images

 


Figure 1. Inverter parasitic view



Figure 2. Your post simulation result

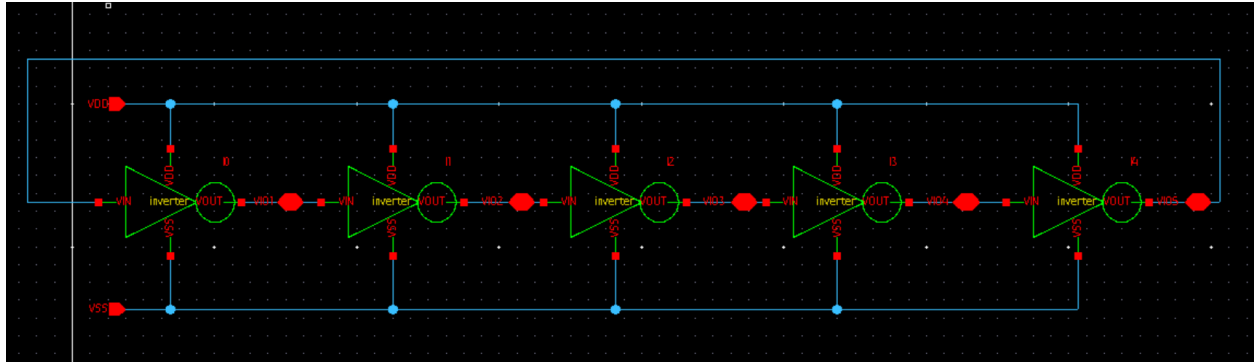


Figure 3. Ring oscillator with Hierarchical design

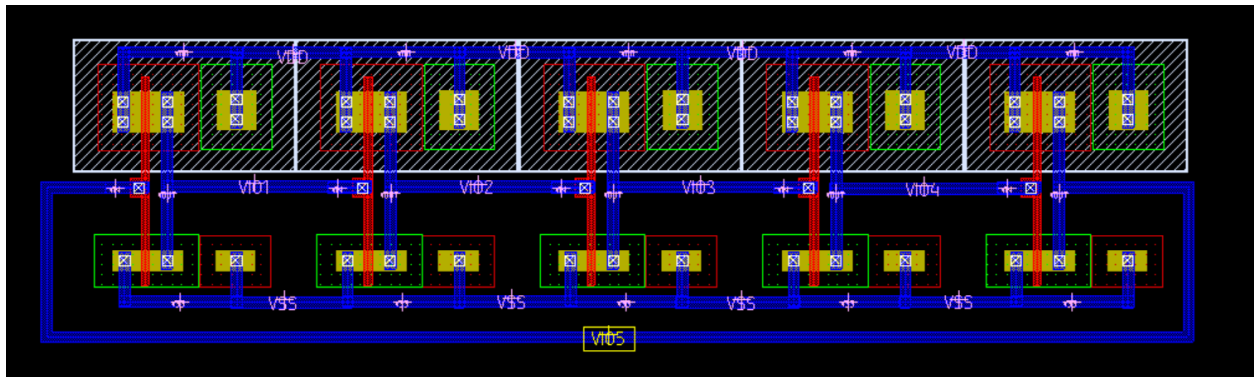


Figure 4. Ring oscillator layout

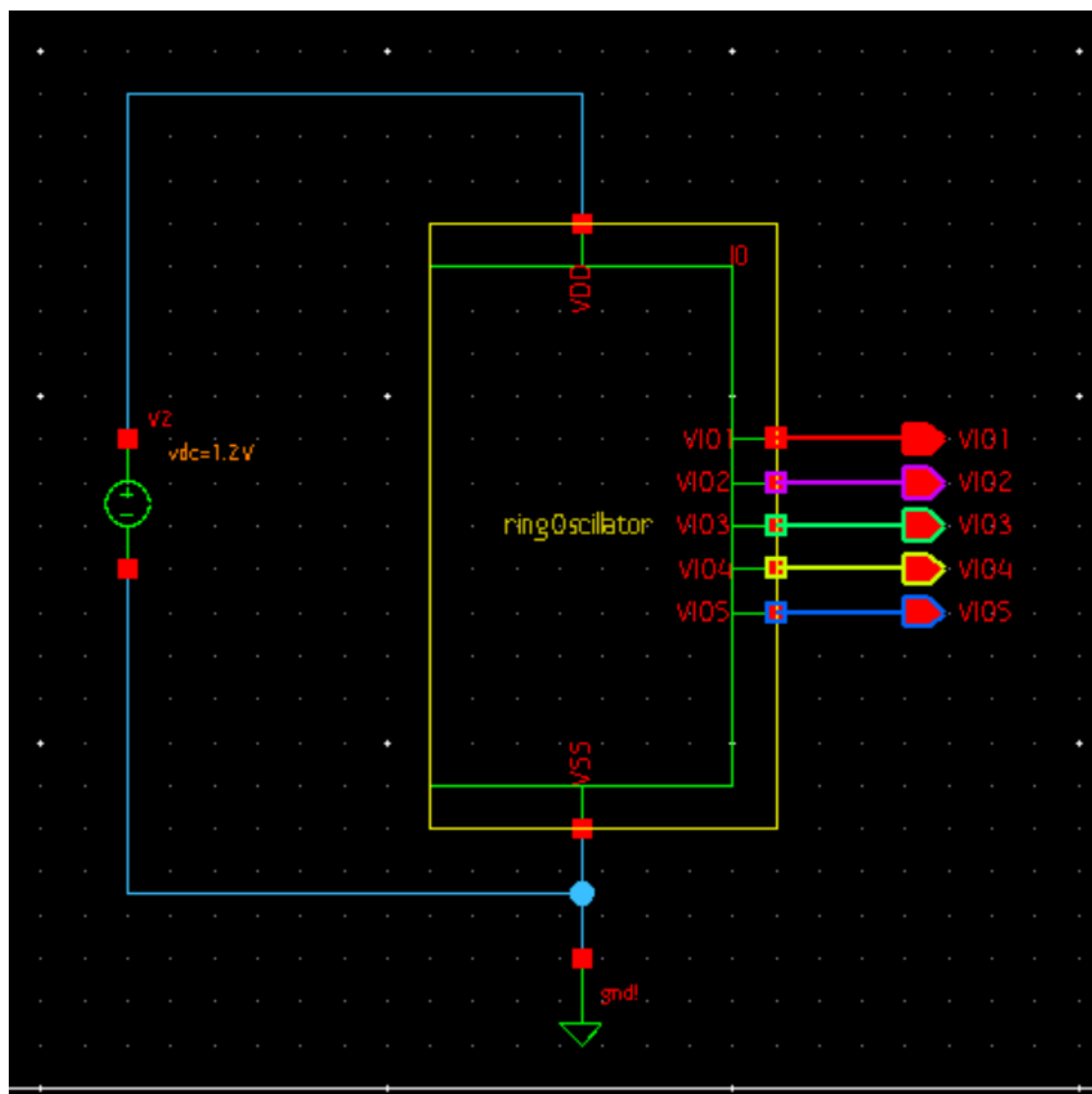


Figure 5. Ring Oscillator Testbench

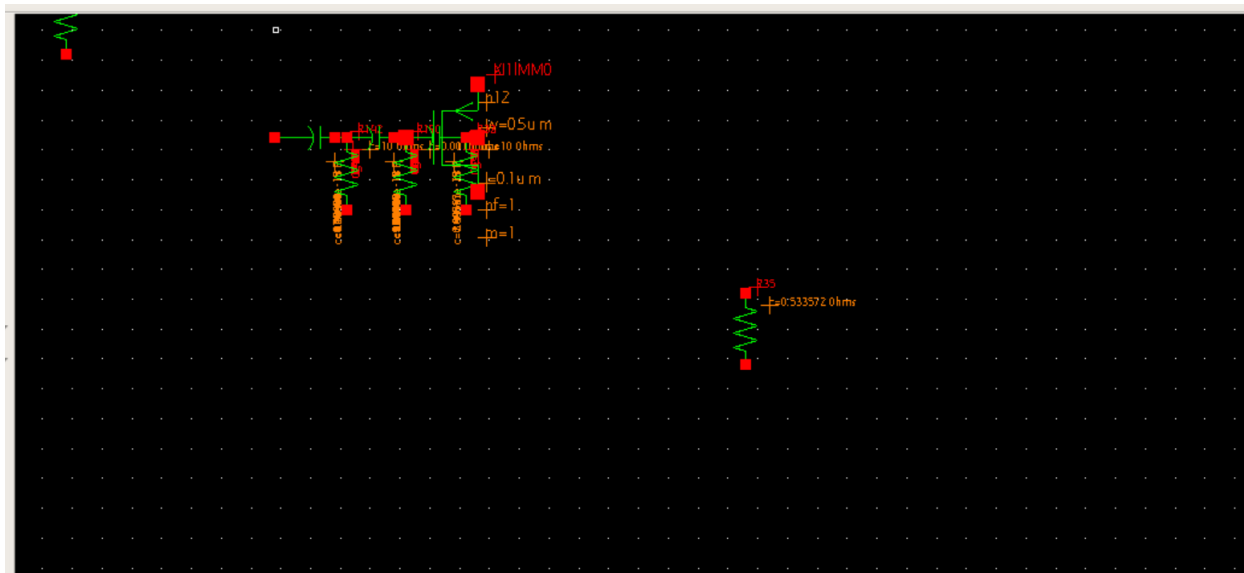


Figure 6. Parasitic Extraction of Ring Oscillator

 


Figure 7. Parasitic Extraction of Ring Oscillator

 


Figure 8. Ring oscillator POST (Layout) SIMULATION result (with parasitic extraction)

## Week 2

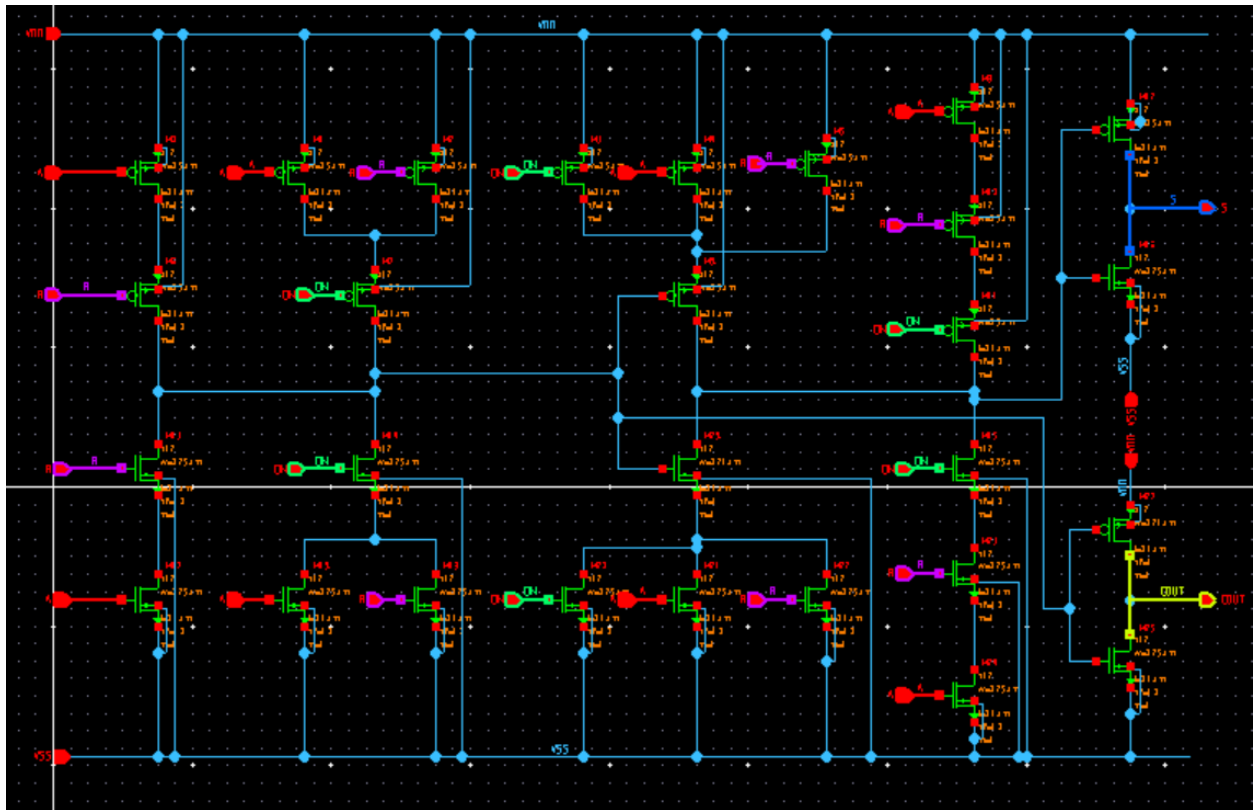


Fig. 9: 1-bit full adder schematic

 


Fig. 10: 1 bit full adder simulation



 


Fig. 11: 1-bit full adder stick diagram

 


Fig. 12: 1-bit full adder layout

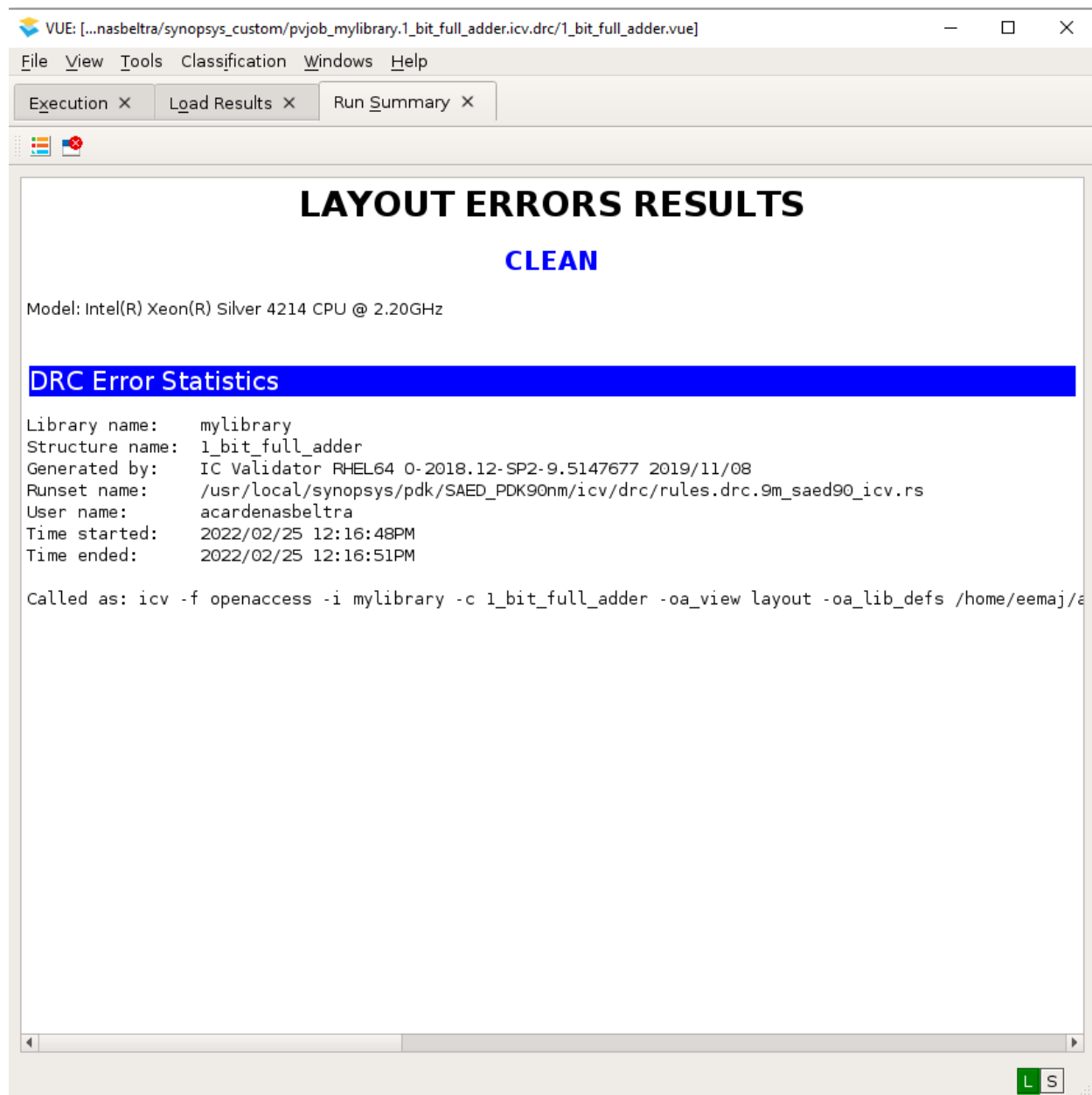


Fig. 13: DRC Result with CLEAN for 1-bit full adder

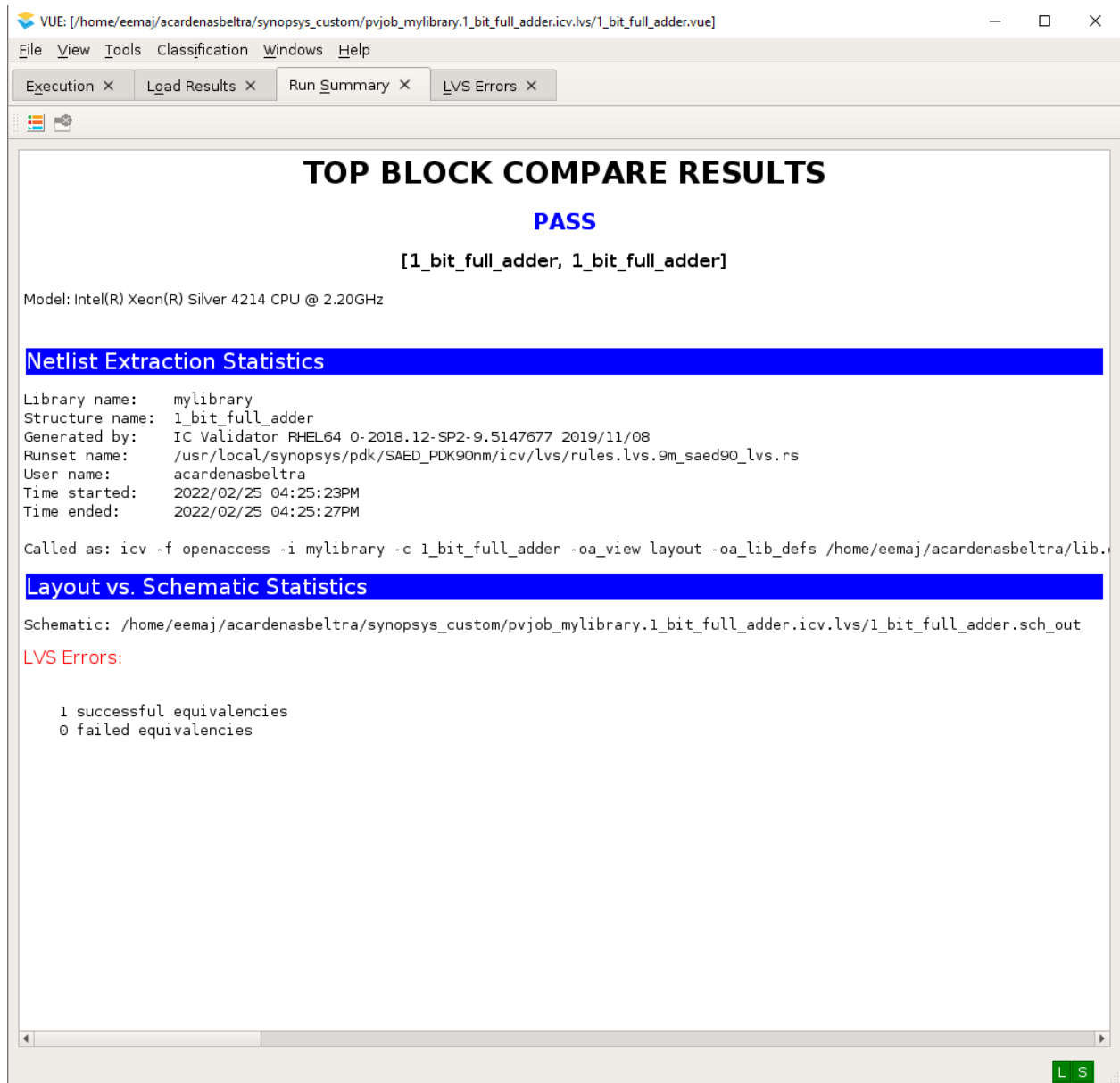


Fig. 14: LVS Result with PASS for 1-bit full adder



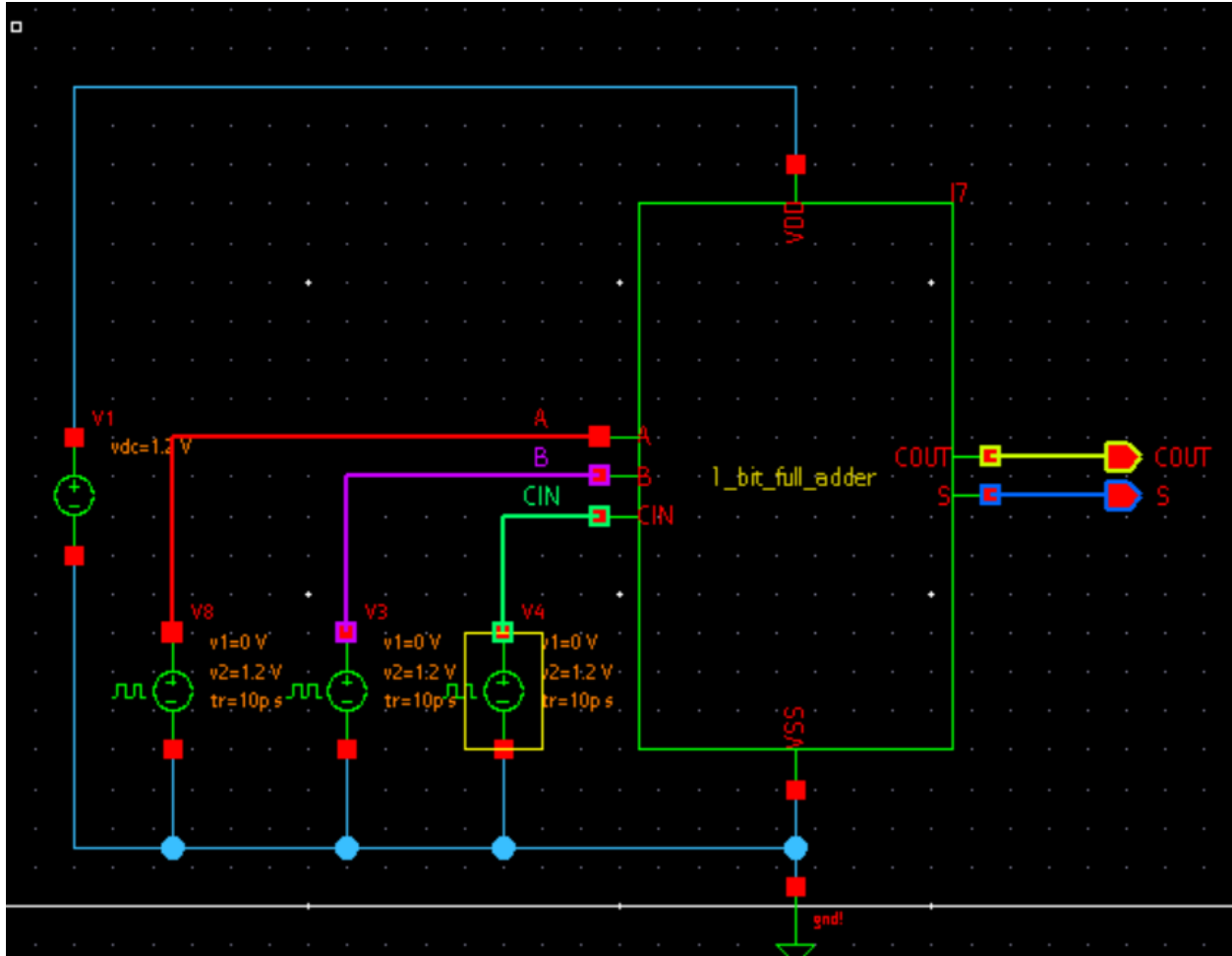


Fig. 16: Fig. 15: 1-bit full adder Post (Layout) Simulation testbench with parasitic extraction

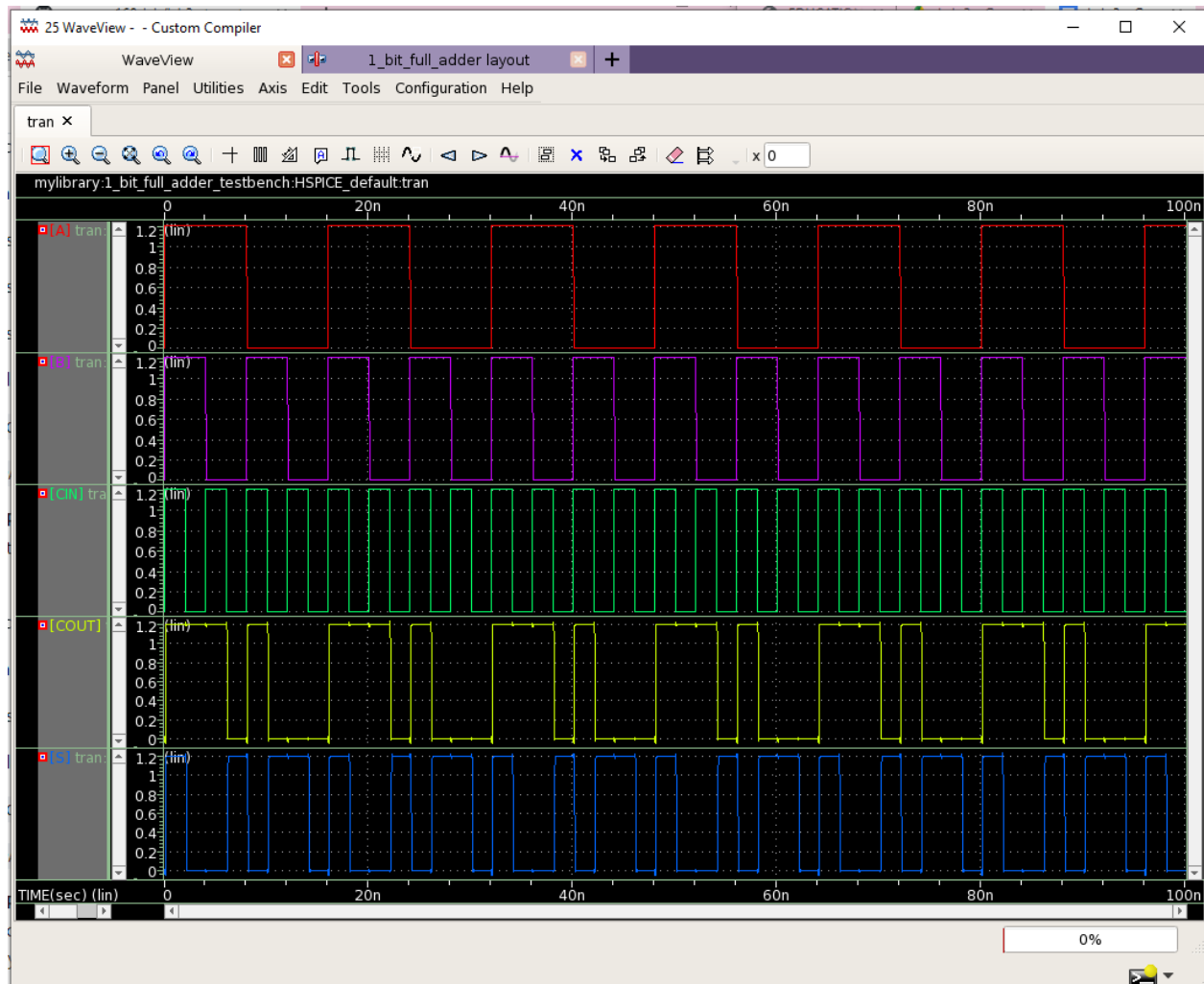


Fig. 17: 1-bit full adder Post (Layout) Simulation result with parasitic extraction

## Week 3

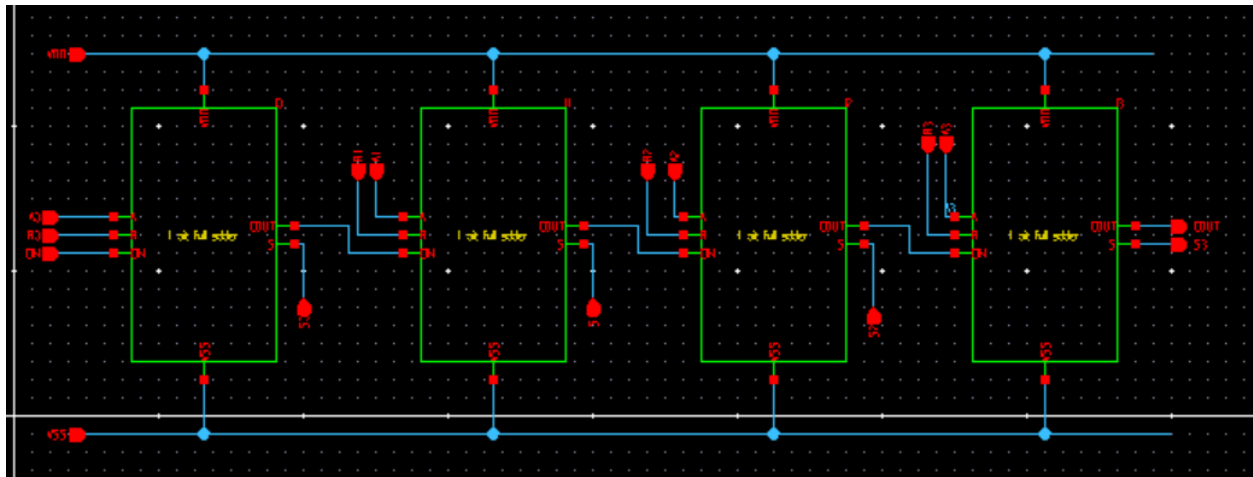


Fig. 18: 4-bit full adder schematic

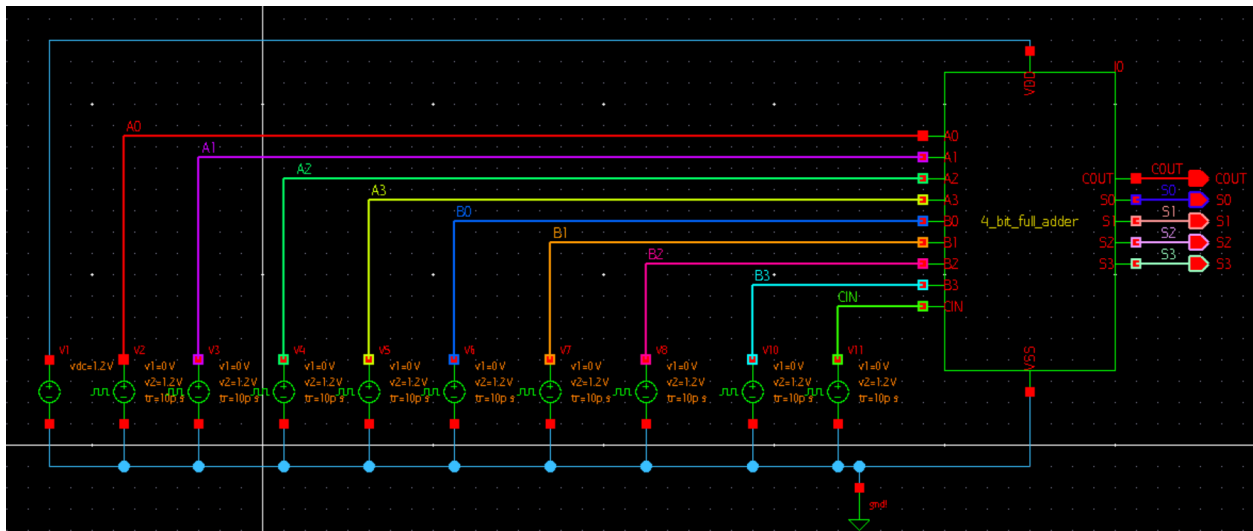


Fig. 19: 4-bit full adder testbench



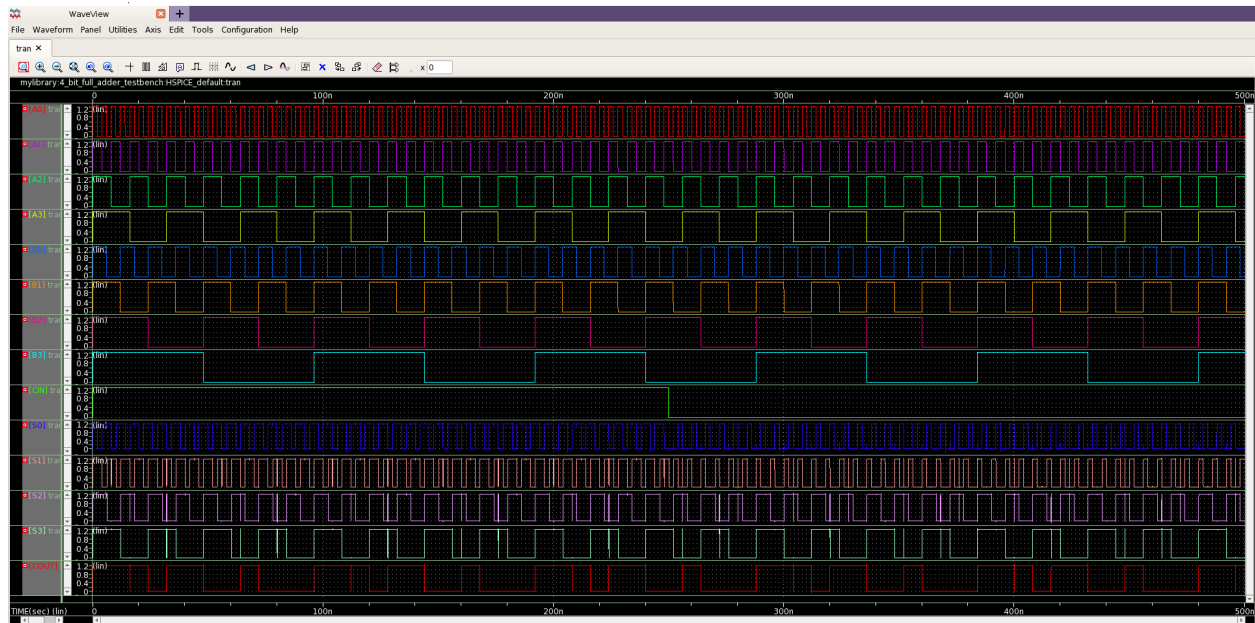


Fig. 19: 4-bit full adder schematic Simulation result

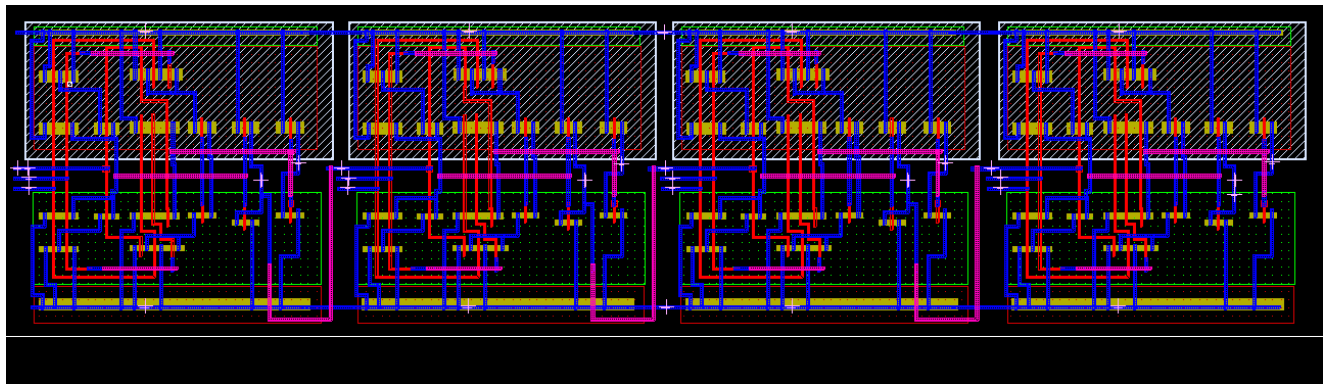


Fig. 20: 4 bit full adder layout

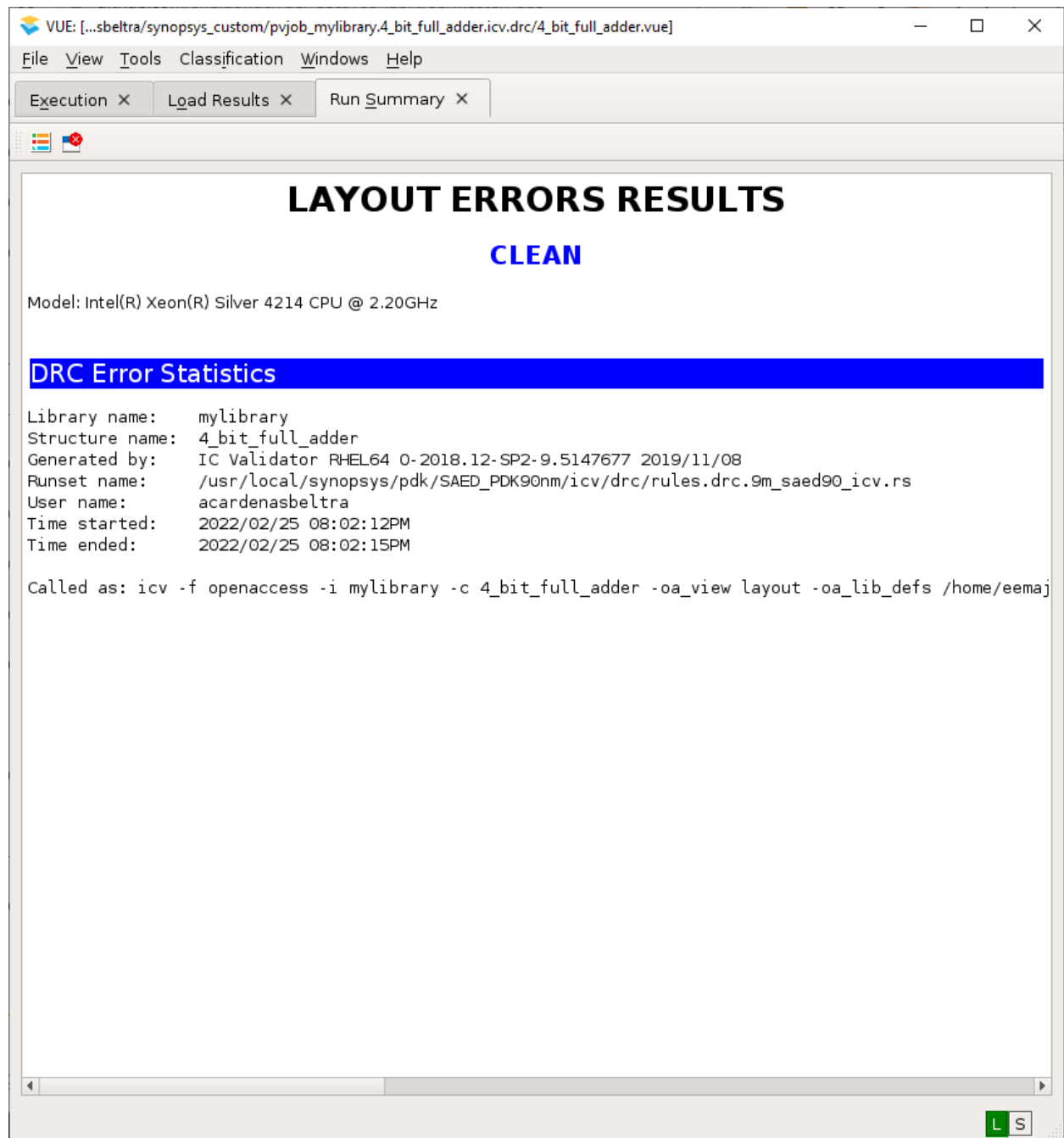


Fig. 21: 4-bit full adder DRC Result

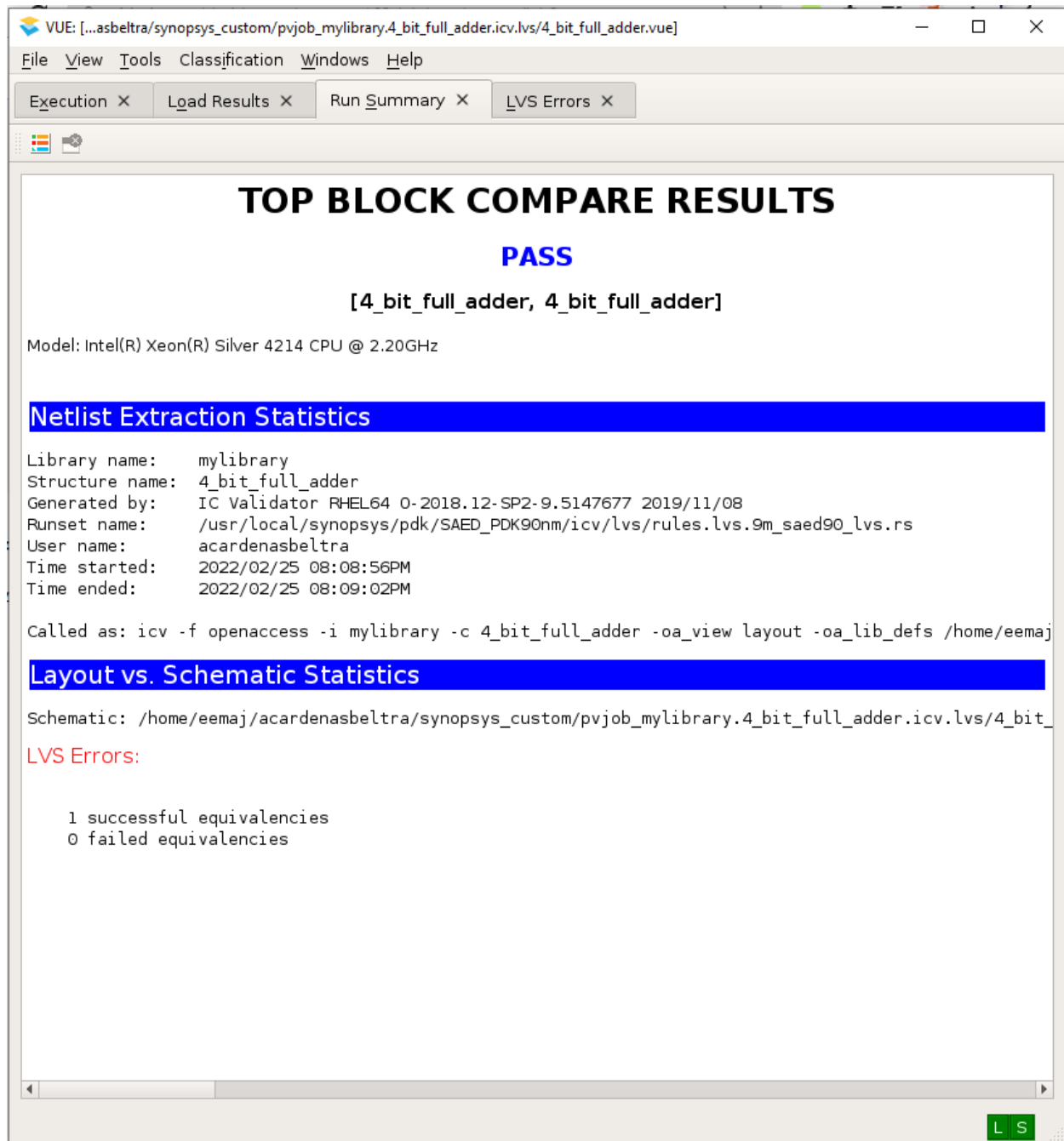


Fig. 22: 4-bit full adder LVS Result

 


Fig. 23: 4-bit full adder Parasitic Extraction

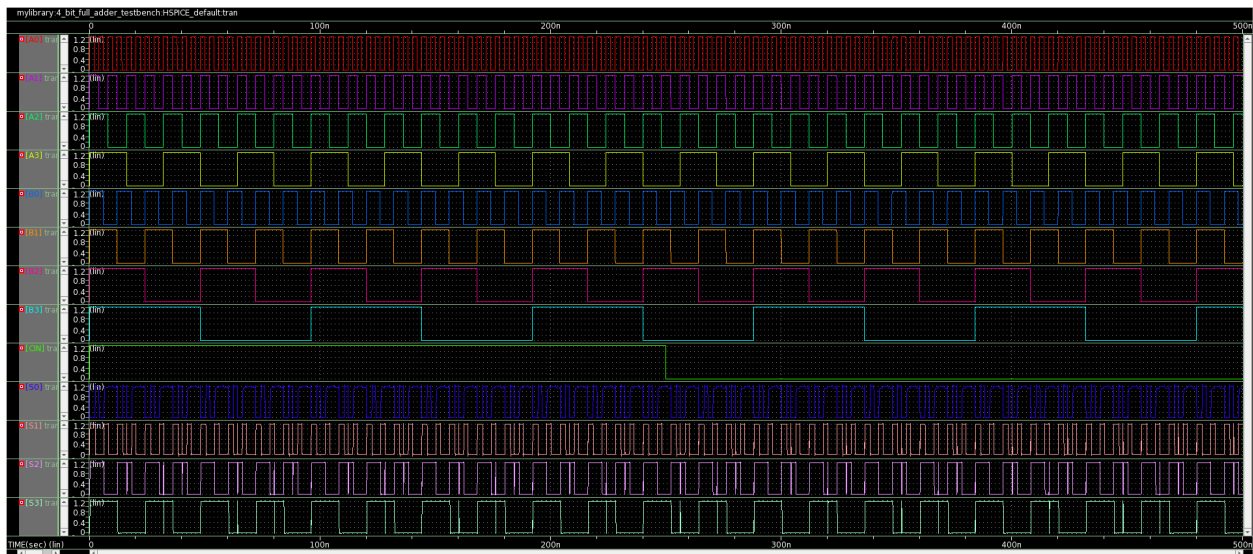


Fig. 23: 4-bit full adder Simulation Result with Parasitic Extraction

## Issues

I had many issues in designing the layout for the 1-bit full adder. I was having trouble visualizing the layout from the circuit schematic. What I did was that in addition to the stick diagram, I drew the layout out on paper. After I had completed my layout, I had many problems with the LVS. One was that I had forgotten to add contacts to the metal of the body of the circuit. Also, My connections for S were separate so I was receiving unmatched errors. After my layout was fully verified, the rest of the lab was fairly simple, but I did spend many hours only on the layout of the 1-bit full adder portion of the lab.